

Primera mallo

•
$$18 = 0.82 I_1 + (I_1 - I_2)$$

 $18 = 1.82 I_1 - I_2$

Segunda malla

Malla 2

•
$$1(I_2 - I_1) + 1,2 I_2 + 2,2 (I_2 - I_3) = 0$$

-I, $4 4,4 I_2 - 2,2 I_3 = 0$

Tercera malla

$$2,2(I_3-I_2) + 0,39I_3 = -5$$

 $-2,2I_2 + 2,59I_3 = -5$

Solucionando el sistema de ecuaciones

$$I_1 = 11, 45 \text{ mA}$$
 $I_2 = 18$
 $I_3 = 0, 48 \text{ mA}$
 $I_4 = 11, 45 \text{ mA}$
 $I_5 = 11, 45 \text{ mA}$
 $I_6 = 11, 45 \text{ mA}$
 $I_7 = 11, 45 \text{ mA}$
 $I_8 = 11, 45 \text{ mA}$

ERROR PORCENTUAL

Malla 1

$$e\% = \frac{V + eonico - V \cdot mudiaol}{V \cdot heonico} \times 100 = 0,35\%$$

$$= \frac{111,50 - 11,451}{1150} \times 100 = 0,43\%$$

Malla 3